

Small Signal Audio Design

Douglas Self



ELSEVIER

AMSTERDAM • BOSTON • HEIDELBERG • LONDON • NEW YORK • OXFORD
PARIS • SAN DIEGO • SAN FRANCISCO • SINGAPORE • SYDNEY • TOKYO

Focal Press is an imprint of Elsevier



Contents

<i>Preface</i>	<i>xiii</i>
<i>About the Author</i>	<i>xvii</i>
<i>Acronyms</i>	<i>xviii</i>
<i>Chapter 1 The Basics</i>	<i>1</i>
Signals.....	1
Amplifiers.....	2
Voltage Amplifiers.....	2
Transconductance Amplifiers.....	2
Current Amplifiers.....	3
Transimpedance Amplifiers.....	3
Negative Feedback.....	4
Nominal Signal Levels.....	5
Gain Structures.....	6
Amplification Then Attenuation.....	6
Attenuation Then Amplification.....	7
Raising the Input Signal to the Nominal Level.....	7
Active Gain Controls.....	8
Noise.....	8
Johnson Noise.....	9
Shot Noise.....	11
$1/f$ Noise (Flicker Noise).....	12
Popcorn Noise.....	13
Summing Noise Sources.....	13
Noise in Amplifiers.....	14
Noise in Bipolar Transistors.....	16
Bipolar Transistor Voltage Noise.....	16
Bipolar Transistor Current Noise.....	17
Noise in JFETs.....	20
Noise in Op-Amps.....	21
Low-Noise Op-Amp Circuitry.....	22
Noise Measurements.....	23
How to Attenuate Quietly.....	23

How to Amplify Quietly.....	25
How to Invert Quietly.....	26
How to Balance Quietly.....	28
Ultra-Low-Noise Design with Multipath Amplifiers.....	28
Ultra-Low-Noise Voltage Buffers.....	29
Ultra-Low-Noise Amplifiers.....	30
References.....	32
<i>Chapter 2 Components.....</i>	<i>33</i>
Conductors.....	33
Copper and Other Conductive Elements.....	34
The Metallurgy of Copper.....	35
Gold and Its Uses.....	35
Cable and Wiring Resistance.....	36
PCB Track Resistance.....	37
PCB Track-to-Track Crosstalk.....	39
Impedances and Crosstalk: A Case History.....	40
Resistors.....	42
Through-Hole Resistors.....	43
Surface-Mount Resistors.....	43
Resistor Imperfections.....	45
Resistor Noise.....	46
Resistor Non-Linearity.....	48
Capacitors.....	51
Capacitor Non-Linearity Examined.....	52
Non-Electrolytic Capacitor Non-Linearity.....	53
Electrolytic Capacitor Non-Linearity.....	58
Inductors.....	61
References.....	61
<i>Chapter 3 Discrete Transistor Circuitry.....</i>	<i>63</i>
Why Use Discrete Transistor Circuitry?.....	63
Bipolars and FETs.....	64
Bipolar Junction Transistors.....	64
The Transistor Equation.....	65
Beta.....	66
Unity-Gain Buffer Stages.....	66
The Simple Emitter-Follower.....	67
The Constant-Current Emitter-Follower.....	70
The Push-Pull Emitter-Follower.....	71
Emitter-Follower Stability.....	72
CFP Emitter-Followers.....	73
Improved Unity-Gain Buffers.....	75
Gain Stages.....	81

One-Transistor Shunt-Feedback Gain Stages.....	81
One-Transistor Series-Feedback Gain Stages.....	82
Two-Transistor Shunt-Feedback Gain Stages.....	82
Two-Transistor Series-Feedback Gain Stages.....	87
Discrete Op-Amp Design.....	88
High-Input-Impedance Bipolar Stages.....	92
References.....	94
Chapter 4 Op-Amps and Their Properties.....	95
A Very Brief History of Op-Amps.....	95
Op-Amp Properties: Noise.....	96
Op-Amp Properties: Slew Rate.....	97
Op-Amp Properties: Common-Mode Range.....	98
Op-Amp Properties: Input Offset Voltage.....	98
Op-Amp Properties: Bias Current.....	99
Op-Amp Properties: Cost.....	100
Op-Amp Properties: Distortion.....	101
Op-Amp Internal Distortion.....	101
Slew-Rate-Limiting Distortion.....	101
Distortion Due to Loading.....	103
Thermal Distortion.....	104
Common-Mode Distortion.....	104
Bipolar input op-amps.....	104
FET op-amps.....	108
Rail bootstrapping to reduce CM distortion.....	110
Simpler rail bootstrapping.....	113
Bootstrapping series-feedback JFET op-amp stages.....	114
Selecting the Right Op-Amp.....	115
Op-Amps Surveyed: BJT Input Types.....	117
The LM741 Op-Amp.....	118
The NE5532/5534 Op-Amp.....	118
Deconstructing the 5532.....	120
The LM4562 Op-Amp.....	121
The AD797 Op-Amp.....	124
The OP27 Op-Amp.....	124
The OP270 Op-Amp.....	125
The OP275 Op-Amp.....	126
Op-Amps Surveyed: JFET Input Types.....	128
The TL072 Op-Amp.....	128
The TL052 Op-Amp.....	129
The OPA2134 Op-Amp.....	131
The OPA604 Op-Amp.....	132
The OPA627 Op-Amp.....	135
References.....	136

<i>Chapter 5 Filters</i>	137
Passive Filters.....	137
Active Filters.....	138
Low-Pass Filters.....	138
High-Pass Filters.....	138
Combined Low-Pass and High-Pass Filters.....	139
Bandpass Filters.....	139
Notch Filters.....	139
All-Pass Filters.....	139
Filter Characteristics.....	140
Sallen-and-Key Filters.....	140
Distortion in Sallen-and-Key Filters.....	145
Multiple-Feedback Bandpass Filters.....	147
Making Notch Filters.....	148
Differential Filters.....	150
References.....	151
 <i>Chapter 6 Preamplifier Architectures</i>	 753
Passive Preamplifiers.....	153
Active Preamplifiers.....	155
Amplification and the gain-distribution problem.....	156
Active Gain Controls.....	158
Recording Facilities.....	158
Tone Controls.....	158
References.....	159
 <i>Chapter 7 Moving-Magnet Disc Inputs</i>	 161
The Vinyl Medium.....	161
Spurious Signals.....	162
Maximum Signal Levels on Vinyl.....	163
Equalization and Its Discontents.....	166
The 'Neumann Pole'.....	168
Implementing RIAA Equalization.....	168
Passive and Semi-Passive RIAA Equalization.....	171
Calculating the RIAA Equalization Components.....	175
RIAA Equalization Component Tolerances.....	175
Simulating Inverse RIAA Equalization.....	178
Physical Inverse RIAA Equalization.....	179
Overload Margins.....	179
Cartridge Impedances.....	181
Cartridge Loading.....	181
Cartridge-Preamplifier Interaction.....	183
Cartridge DC and AC Coupling.....	183

Discrete MM Disc Input Stages.....	183
Op-Amp MM Disc Input Stages.....	187
Noise in RIAA Preamplifiers.....	191
Noise Results with A-Weighting.....	196
RIAA Noise Measurements.....	196
Electronic Cartridge Loading for Lower Noise.....	197
Subsonic Filters.....	201
Combining Subsonic and Ultrasonic Filters.....	204
References.....	204
Chapter 8 Moving-Coil Head Amplifiers.....	207
Moving-Coil Cartridge Characteristics.....	207
Amplification Strategies.....	208
Moving-Coil Transformers.....	209
Moving-Coil Input Amplifiers.....	210
A New Moving-Coil Amplifier Configuration.....	213
The Complete Circuit.....	216
Performance.....	216
References.....	218
Chapter 9 Volume and Balance Controls.....	279
Volume Controls.....	219
Volume Control Laws.....	220
Loaded Linear Pots.....	221
Dual-Action Volume Controls.....	223
Tapped Volume Controls.....	226
Slide Faders.....	229
Active Volume Controls.....	231
The Baxandall Active Volume Control.....	235
A Practical Baxandall Active Gain Stage.....	237
Potentiometers and DC.....	238
Motorized Potentiometers.....	239
Stepped Volume Controls.....	240
Switched Attenuator Volume Controls.....	241
Relay-Switched Volume Controls.....	249
Transformer-Tap Volume Controls.....	250
Integrated Circuit Volume Controls.....	250
Balance Controls: Passive.....	250
Active Balance Controls.....	252
Mono/Stereo Switches.....	254
Width Controls.....	254
References.....	255

<i>Chapter 10 Tone Controls and Equalizers</i>	257
Passive Tone Controls.....	258
Baxandall Tone Controls.....	259
The Baxandall Two-Capacitor LF Control.....	260
The Baxandall Two-Capacitor Tone Control.....	263
The Baxandall Two-Capacitor HF Control.....	265
¹ Switched-Frequency Baxandall Controls.....	266
Variable-Frequency LF and HF EQs.....	267
Tone-Balance Controls.....	269
Middle Controls.....	271
Fixed-Frequency Baxandall Middle Controls.....	271
Three-Band Baxandall EQ in One Stage.....	273
Wien Fixed Middle EQ.....	276
Sweep Middles.....	276
The Single-Gang Sweep Middle.....	278
Switched-Q Variable-Frequency Wien Middle EQs.....	280
Switchable Peak/Shelving LF/HF EQs.....	281
Parametric Middle EQs.....	283
Graphic Equalizers.....	286
References.....	289
 <i>Chapter 11 A Complete Preamplifier</i>	 297
Architecture and Philosophy.....	291
The Line Inputs.....	293
The High-Impedance Input Buffer.....	293
The Tone-Control Stage.....	294
The Active Gain Stage.....	300
Performance.....	301
References.....	302
 <i>Chapter 12 Mixer Architectures</i>	 303
Performance Factors.....	303
Mixer Internal Levels.....	304
Mixer Architecture.....	305
The Split Mixing Architecture.....	306
The In-Line Mixing Architecture.....	308
A Closer Look at Split-Format Modules.....	310
The Channel Module (Split Format).....	310
Effects Return Modules.....	313
The Group Module.....	314
The Master Module.....	316
Talkback and Oscillator Systems.....	317
The In-Line Channel Module.....	319

<i>Chapter 13 Microphone Preamplifiers</i>	323
Microphone Preamplifier Requirements.....	323
Transformer Microphone Inputs.....	324
The Simple Hybrid Microphone Preamplifier.....	325
The Balanced-Feedback Hybrid Microphone Preamplifier.....	326
Microphone and Line-Input Pads.....	329
The Padless Microphone Preamplifier.....	331
Capacitor Microphone Head Amplifiers.....	335
 <i>Chapter 14 Line Inputs</i>	339
External Signal Levels.....	339
Internal Signal Levels.....	339
Input Amplifier Functions.....	340
Unbalanced Inputs.....	340
Balanced Interconnections.....	344
The Advantages of Balanced Interconnections.....	345
The Disadvantages of Balanced Interconnections.....	345
Balanced Cables and Interference.....	346
Electrostatic Coupling.....	346
Magnetic Coupling.....	347
Ground Voltages.....	348
Balanced Connectors.....	348
Balanced Signal Levels.....	348
Electronic vs. Transformer Balanced Inputs.....	349
Common-Mode Rejection.....	349
The Basic Electronic Balanced Input.....	352
Common-Mode Rejection: The Basic Balanced Input and Op-Amp Effects.....	354
Op-Amp Frequency Response Effects.....	355
Op-Amp CMRR Effects.....	357
Amplifier Component Mismatch Effects.....	357
A Practical Balanced Input.....	359
Variations on the Balanced Input Stage.....	362
Combined Unbalanced and Balanced Inputs.....	362
The Superbal Input.....	363
Switched-Gain Balanced Inputs.....	364
Variable-Gain Balanced Inputs.....	365
High-Input-Impedance Balanced Inputs.....	366
The Inverting Two-Op-Amp Input.....	367
The Instrumentation Amplifier.....	368
Transformer Balanced Inputs.....	370
Input Overvoltage Protection.....	371
Low-Noise Balanced Inputs.....	372
Low-Noise Balanced Inputs in Real Life.....	377

Ultra-Low-Noise Balanced Inputs.....	378
References.....	380
<i>Chapter 15 Line Outputs.....</i>	<i>381</i>
Unbalanced Outputs.....	381
Zero-Impedance Outputs.....	382
Ground-Canceling Outputs.....	383
Balanced Outputs.....	386
Quasi-Floating Outputs.....	386
Transformer Balanced Outputs.....	388
Driving Heavy Loads.....	389
Reference.....	392
<i>Chapter 16 Signal Switching.....</i>	<i>393</i>
Mechanical Switches.....	393
Input-Select Switching.....	394
The Virtual Contact.....	395
Relay Switching.....	397
Electronic Switching.....	397
Switching with CMOS Analog Gates.....	397
CMOS Gates in Voltage Mode.....	399
CMOS Gates in Current Mode.....	404
Series-Shunt Current Mode.....	406
Control Voltage Feedthrough in CMOS Gates.....	407
Discrete JFET Switching.....	407
JFETs in Voltage Mode: The Series JFET Switch.....	408
The Shunt JFET Switch in Voltage Mode.....	413
JFETs in Current Mode.....	414
Reducing Distortion by Biasing.....	417
JFET Drive Circuitry.....	418
Physical Layout and Offness.....	419
Dealing with the DC Conditions.....	420
A Soft Changeover Circuit.....	420
Control-voltage feedthrough in JFETs.....	421
Reference.....	421
<i>Chapter 17 Mixer Subsystems.....</i>	<i>423</i>
Mixer Bus Systems.....	423
Input Anangements.....	424
Equalization.....	424
Insert Points.....	424
How to Move a Circuit Block.....	426
Faders.....	428
Postfade Amplifiers.....	428

Direct Outputs.....	430
Panpots.....	431
Passive Panpots.....	432
The Active Panpot.....	438
LCR Panpots.....	439
Routing Systems.....	442
Auxiliary Sends.....	446
Group Module Circuit Blocks.....	446
Summing Systems.....	447
Voltage Summing.....	447
Virtual-Earth Summing.....	448
Balanced Summing Systems.....	449
Ground-Canceling Summing Systems.....	451
Distributed Summing Systems.....	452
Summing Amplifiers.....	456
Hybrid Summing Amplifiers.....	459
Balanced Hybrid Summing Amplifiers.....	462
PFL Systems.....	465
PFL Summing.....	466
PFL Switching.....	466
PFL Detection.....	468
Virtual-Earth PFL Detection.....	469
AFL Systems.....	471
Solo-in-Place Systems.....	473
Talkback Microphone Amplifiers.....	473
Line-Up Oscillators.....	474
Console Cooling and Component Lifetimes.....	477
 <i>Chapter 18 Level Indication and Metering.....</i>	 479
Signal-Present Indication.....	479
Peak Indication.....	479
Distributed Peak Detection.....	481
Combined LED Indicators.....	483
VU Meters.....	483
PPM Meters.....	485
LED Bar-Graph Metering.....	486
A More Efficient LED Bar-Graph Architecture.....	488
Vacuum Fluorescent Displays.....	491
LCD Meter Displays.....	491
 <i>Chapter 19 Level Control and Special Circuits.....</i>	 493
Gain-Control Elements.....	493
A Brief History.....	493
JFETs.....	493

Operational Transconductance Amplifiers.....	496
Voltage-Controlled Amplifiers.....	497
Compressors and Limiters.....	499
Attack Artefacts.....	503
Decay Artefacts.....	504
Subtractive VCA Control.....	505
Noise Gates.....	506
Clipping.....	508
Diode Clipping.....	508
Active Clipping with Transistors.....	510
Active Clipping with Op-Amps.....	512
Noise Generators.....	521
Pinkening Filters.....	523
References.....	524
Chapter 20 Power Supplies.....	525
Op-Amp Supply-Rail Voltages.....	525
Designing a ± 15 V Supply.....	527
Designing a ± 17 V Supply.....	529
Using Variable-Voltage Regulators.....	531
Improving Ripple Performance.....	532
Dual Supplies From a Single Winding.....	533
Power Supplies for Discrete Circuitry.....	534
Larger Power Supplies.....	534
Mutual Shutdown Circuitry.....	536
Very Large Power Supplies.....	536
Microcontroller and Relay Supplies.....	537
+48 V Phantom Power Supplies.....	538
Reference.....	540
Chapter 21 Interfacing with the Digital Domain.....	547
PCB Layout Considerations.....	541
Nominal Levels and ADCs.....	542
Some Typical ADCs.....	543
Interfacing with ADC Inputs.....	544
Some Typical DACs.....	546
Interfacing with DAC Outputs.....	547
Index.....	549