

# **ELECTRIC POWER PRINCIPLES**

## **Sources, Conversion, Distribution and Use**

James L. Kirtley

*Massachusetts Institute of Technology, USA*

**WILEY**

A John Wiley and Sons, Ltd., Publication

# Contents

<b>Preface</b>	<b>xi</b>
<b>1 Electric Power Systems</b>	<b>1</b>
1.1 Electric Utility Systems	2
1.2 Energy and Power	3
1.2.1 <i>Basics and Units</i>	3
1.3 Sources of Electric Power	3
1.3.1 <i>Heat Engines</i>	4
1.3.2 <i>Power Plants</i>	5
1.3.3 <i>Nuclear Power Plants</i>	8
1.3.4 <i>Hydroelectric Power</i>	9
1.3.5 <i>Wind Turbines</i>	10
1.3.6 <i>Solar Power Generation</i>	12
1.4 Electric Power Plants and Generation	15
1.5 Problems	15
<b>2 AC Voltage, Current and Power</b>	<b>17</b>
2.1 Sources and Power	17
2.1.1 <i>Voltage and Current Sources</i>	17
2.1.2 <i>Power</i>	18
2.1.3 <i>Sinusoidal Steady State</i>	18
2.1.4 <i>Phasor Notation</i>	19
2.1.5 <i>Real and Reactive Power</i>	19
2.2 Resistors, Inductors and Capacitors	21
2.2.1 <i>Reactive Power and Voltage</i>	22
2.2.2 <i>Reactive Power Voltage Support</i>	23
2.3 Problems	26
<b>3 Transmission Lines</b>	<b>31</b>
3.1 Modelir12: Teleeraoher's Equations	32
3.1.1 <i>Traveling Waves</i>	33
3.1.2 <i>Characteristic Impedance</i>	33
3.1.3 <i>Power</i>	35
3.1.4 <i>Line Terminations and Reflections</i>	35

3.2	<i>3.1.5 Sinusoidal Steady State Problems</i>	40 42
<b>4</b>	<b>Polyphase Systems</b>	<b>45</b>
4.1	<i>4.0.7 Two-Phase Systems Three-Phase Systems</i>	45 47
4.2	<i>4.2.1 Example: Wye and Delta Connected Loads Line-Line Voltages</i>	49 50
4.3	<i>4.2.2 Example: Use of Wye-Delta for Unbalanced Loads Problems</i>	52 54
	▼	
<b>5</b>	<b>Electrical 1 and Magnetic Circuits</b>	<b>57</b>
5.1	<i>5.1.1 Kirchoff's Current Law (KCL) Electric Circuits</i>	57 57
	<i>5.1.2 Kirchoff's Voltage Law (KVL)</i>	58
	<i>5.1.3 Constitutive Relationship: Ohm's Law</i>	58
5.2	<i>5.2.1 Magnetic Circuit Analogies</i>	60
	<i>5.2.2 Analogy to KCL</i>	60
	<i>5.2.3 Analogy to KVL: Magnetomotive Force</i>	61
	<i>5.2.4 Analogy to Ohm's Law: Reluctance</i>	61
	<i>5.2.5 Simple Case</i>	62
	<i>5.2.6 Flux Confinement</i>	63
	<i>5.2.7 Example: C-Core</i>	63
	<i>5.2.8 Example: Core with Different Gaps</i>	64
5.3	<i>Problems</i>	66
<b>6</b>	<b>Transformers</b>	<b>71</b>
6.1	<i>6.1.1 Single-Phase Transformers Ideal Transformer</i>	71 72
	<i>6.1.2 Deviations from Ideal Transformer</i>	73
6.2	<i>6.2.1 Three-Phase Transformers Example</i>	75 77
6.3	<i>Problems</i>	80
<b>7</b>	<b>Polyphase Lines and Single-Phase Equivalents</b>	<b>85</b>
7.1	<i>7.1.1 Polyphase Transmission and Distribution Lines Example</i>	85 87
7.2	<i>7.2.1 Introduction To Per-Unit Systems Normalization Of Voltage and Current</i>	88
	<i>7.2.2 Three-Phase Systems</i>	88
	<i>7.2.3 Networks with Transformers</i>	90
	<i>7.2.4 Transforming from one base to another</i>	90
	<i>7.2.5 Example: Fault Study</i>	91
7.3	<i>7.3.1 Appendix: Inductances of Transmission Lines Single Wire</i>	92 94
	<i>7.3.2 Mutual Inductance</i>	94 96

## Contents

7.3.3	<i>Bundles of Conductors</i>	96
7.3.4	<i>Transposed Lines</i>	97
7.4	Problems	98
<b>8</b>	<b>Electromagnetic Forces and Loss Mechanisms</b>	<b>103</b>
8.1	Energy Conversion Process	103
8.1.1	<i>Principle of Virtual Work</i>	104
8.1.2	<i>Coenergy</i>	108
8.2	Continuum Energy Flow	110
8.2.1	<i>Material Motion</i>	111
8.2.2	<i>Additional Issues in Energy Methods</i>	112
8.2.3	<i>Electric Machine Description</i>	116
8.2.4	<i>Field Description of Electromagnetic Force: The Maxwell Stress Tensor</i>	118
8.2.5	<i>Tying the MST and Poynting Approaches together</i>	120
8.3	Surface Impedance of Uniform Conductors	124
8.3.1	<i>Linear Case</i>	124
8.3.2	<i>Iron</i>	128
8.3.3	<i>Magnetization</i>	128
8.3.4	<i>Saturation and Hysteresis</i>	129
8.3.5	<i>Conduction, Eddy Currents and Laminations</i>	131
8.3.6	<i>Eddy Currents in Saturating Iron</i>	133
8.4	Semi-Empirical Method of Handling Iron Loss	136
8.5	Problems	139
<b>9</b>	<b>Synchronous Machines</b>	<b>145</b>
9.1	Round Rotor Machines: Basics	146
9.1.1	<i>Operation with a Balanced Current Source</i>	147
9.1.2	<i>Operation with a Voltage Source</i>	147
9.2	Reconciliation of Models	150
9.2.1	<i>Torque Angles</i>	150
9.3	Per-Unit Systems	151
9.4	Normal Operation	152
9.4.1	<i>Capability Diagram</i>	153
9.4.2	<i>Vee Curve</i>	153
9.5	Salient Pole Machines: Two-Reaction Theory	154
9.6	Synchronous Machine Dynamics	157
9.7	Synchronous Machine Dynamic Model	159
9.7.1	<i>Electromagnetic Model</i>	159
9.7.2	<i>Park's Equations</i>	160
9.7.3	<i>Power and Torque</i>	164
9.7.4	<i>Per- Unit Normalization</i>	164
9.7.5	<i>Equivalent Circuits</i>	167
9.7.6	<i>Transient Reactances and Time Constants</i>	168
9.8	Statement of Simulation Model	169
9.8.1	<i>Example: Transient Stability</i>	170

9.8.2	<i>Equal Area Transient Stability Criterion</i>	170
9.9	Appendix: Transient Stability Code	173
9.10	Appendix: Winding Inductance Calculation	176
9.70.7	<i>Pitch Factor</i>	180
9.70.2	<i>Breadth Factor</i>	180
9.11	Problems	182
<b>10</b>	<b>System Analysis and Protection</b>	<b>185</b>
10.1	The Symmetrical Component Transformation	185
10.2	Sequence Impedances	188
10.2.1	<i>Balanced Transmission Lines</i>	188
70.2.2	<i>Balanced Load</i>	189
70.2.3	<i>Possibly Unbalanced Loads</i>	190
70.2.4	<i>Unbalanced Sources</i>	191
70.2.5	<i>Rotating Machines</i>	193
70.2.6	<i>Transformers</i>	193
10.3	Fault Analysis	197
10.3.1	<i>Single Line-neutral Fault</i>	198
70.5.2	<i>Double Line-neutral Fault</i>	199
10.3.3	<i>Line-Line Fault</i>	200
10.3.4	<i>Example of Fault Calculations</i>	201
10.4	System Protection	205
70.4.7	<i>Fuses</i>	206
10.5	Switches	-
10.6	Coordination	208
10.6.1	<i>Ground Overcurrent</i>	208
10.7	Impedance Relays	208
70.7.7	<i>Directional Elements</i>	209
10.8	Differential Relays	210
10.8.1	<i>Ground Fault Protection for Personnel</i>	211
10.9	Zones of System Protection	212
10.10	Problems	212
<b>11</b>	<b>Load Flow</b>	<b>219</b>
11.1	Two Ports and Lines	219
77.7.7	<i>Power Circles</i>	221
11.2	Load Flow in a Network	222
11.3	Gauss-Seidel Iterative Technique	224
11.4	Bus Admittance	226
11.4.1	<i>Bus Incidence</i>	226
11.4.2	<i>Alternative Assembly of Bus Admittance</i>	227
11.5	Example: Simple Program	228
11.5.1	<i>Example Network</i>	228
11.6	MATLAB Script for the Load How Example	229
11.7	Problems	231

<b>12</b>	<b>Power Electronics and Converters in Power Systems</b>	<b>235</b>
12.1	Switching Devices	235
	72.7.7 <i>Diode</i>	236
	12.1.2 <i>Thyristor</i>	236
	12.1.3 <i>Bipolar Transistors</i>	237
12.2	Rectifier Circuits	239
	72.2.7 <i>Full-Wave Rectifier</i>	239
12.3	DC-DC Converters	247
	72.3.7 <i>Pulse Width Modulation</i>	249
	12.3.2 <i>Boost Converter</i>	249
12.4	Canonical Cell	255
	12.4.1 <i>Bidirectional Converter</i>	255
	12.4.2 <i>H-Bridge</i>	257
12.5	Three-Phase Bridge Circuits	259
	12.5.1 <i>Rectifier Operation</i>	259
	12.5.2 <i>Phase Control</i>	261
	12.5.3 <i>Commutation Overlap</i>	262
	12.5.4 <i>AC Side Current Harmonics</i>	265
12.6	High-Voltage DC Transmission	270
12.7	Basic Operation of a Converter Bridge	271
	72.7.7 <i>Turn-On Switch</i>	272
	12.7.2 <i>Inverter Terminal</i>	272
12.8	Achieving High Voltage	273
12.9	Problems	274
<b>13</b>	<b>Induction Machines</b>	<b>281</b>
13.1	Introduction	281
13.2	Induction Machine Transformer Model	283
	13.2.1 <i>Operation: Energy Balance</i>	289
	13.2.2 <i>Example of Operation</i>	294
	13.2.3 <i>Motor Performance Requirements</i>	294
13.3	Squirrel-Cage Machines	296
13.4	Single-Phase Induction Motors	297
	73.4.7 <i>Rotating Fields</i>	297
	13.4.2 <i>Power Conversion in the Single-Phase Induction Machine</i>	298
	13.4.3 <i>Starting of Single-Phase Induction Motors</i>	300
	73.4.4 <i>Split Phase Operation</i>	301
13.5	Induction Generators	303
13.6	Induction Motor Control	306
	73.6.7 <i>Volts/Hz Control</i>	306
	73.6.2 <i>Field Oriented Control</i>	307
	73.6.3 <i>Elementary Model</i>	308
	73.6.4 <i>Simulation Model</i>	309
	73.6.5 <i>Control Model</i>	310
	73.6.6 <i>Field-Oriented Strategy</i>	311

13.7	Doubly Fed Induction Machines	313
	73.7.7 <i>Steady State Operation</i>	315
13.8	Appendix 1: Squirrel-Cage Machine Model	318
	13.8.1 <i>Rotor Currents and Induced Flux</i>	319
	73.8.2 <i>Squirrel-Cage Currents</i>	320
13.9	Appendix 2: Single-Phase Squirrel Cage Model	325
13.10	Appendix 3: Induction Machine Winding Schemes	326
	13.10.1 <i>Winding Factor for Concentric Windings</i>	329
13.11	Problems	331
<b>14</b>	<b>DC (Commutator) Machines</b>	<b>337</b>
14.1	Geometry	337
14.2	Torque Production	338
14.3	Back Voltage	339
14.4	Operation	341
	74.4.7 <i>Shunt Operation</i>	342
	14.4.2 <i>Separately Excited</i>	343
	74.4.3 <i>Machine Capability</i>	345
14.5	Series Connection	346
14.6	Universal Motors	348
14.7	Commutator	349
	74.7.7 <i>Commutation Interpoles</i>	351
	74.7.2 <i>Compensation</i>	351
14.8	Compound Wound DC Machines	352
14.9	Problems	354
<b>15</b>	<b>Permanent Magnets in Electric Machines</b>	<b>357</b>
15.1	Permanent Magnets	357
	75.7.7 <i>Permanent Magnets in Magnetic Circuits</i>	359
	75.7.2 <i>Load Line Analysis</i>	360
15.2	Commutator Machines	363
	75.2.7 <i>Voltage</i>	365
	75.2.2 <i>Armature Resistance</i>	366
15.3	Brushless PM Machines	367
15.4	Motor Morphologies	367
	75.4.7 <i>Surface Magnet Machines</i>	367
	75.4.2 <i>Interior Magnet, Flux Concentrating Machines</i>	368
	75.4.3 <i>Operation</i>	369
	75.4.4 <i>A Little Two-Reaction Theory</i>	371
	75.4.5 <i>Finding Torque Capability</i>	374
15.5	Problems	380
<b>Index</b>		<b>385</b>